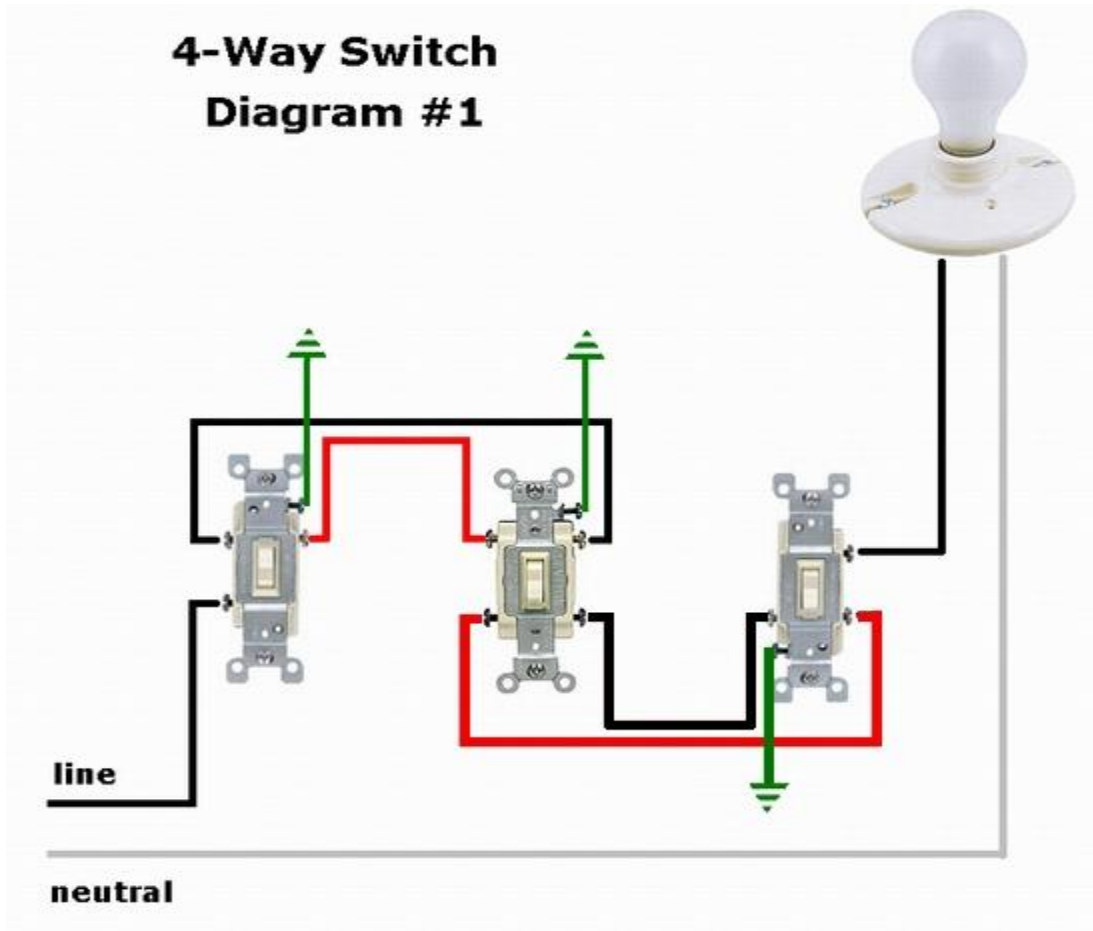


Four Way Switch Lab #1

Electricity

Using the diagram below wire the light receptacle to the switches.




Evaluation Score Card

	Possible	Earned	Points
Correct Switch	5	_____	
Correct wires	5	_____	
Properly tightened	5	_____	
Project is straight and neatly constructed	3	_____	
Safe work habits	2	_____	
Total	20	_____	

Four Way Switch Lab #2

Electricity

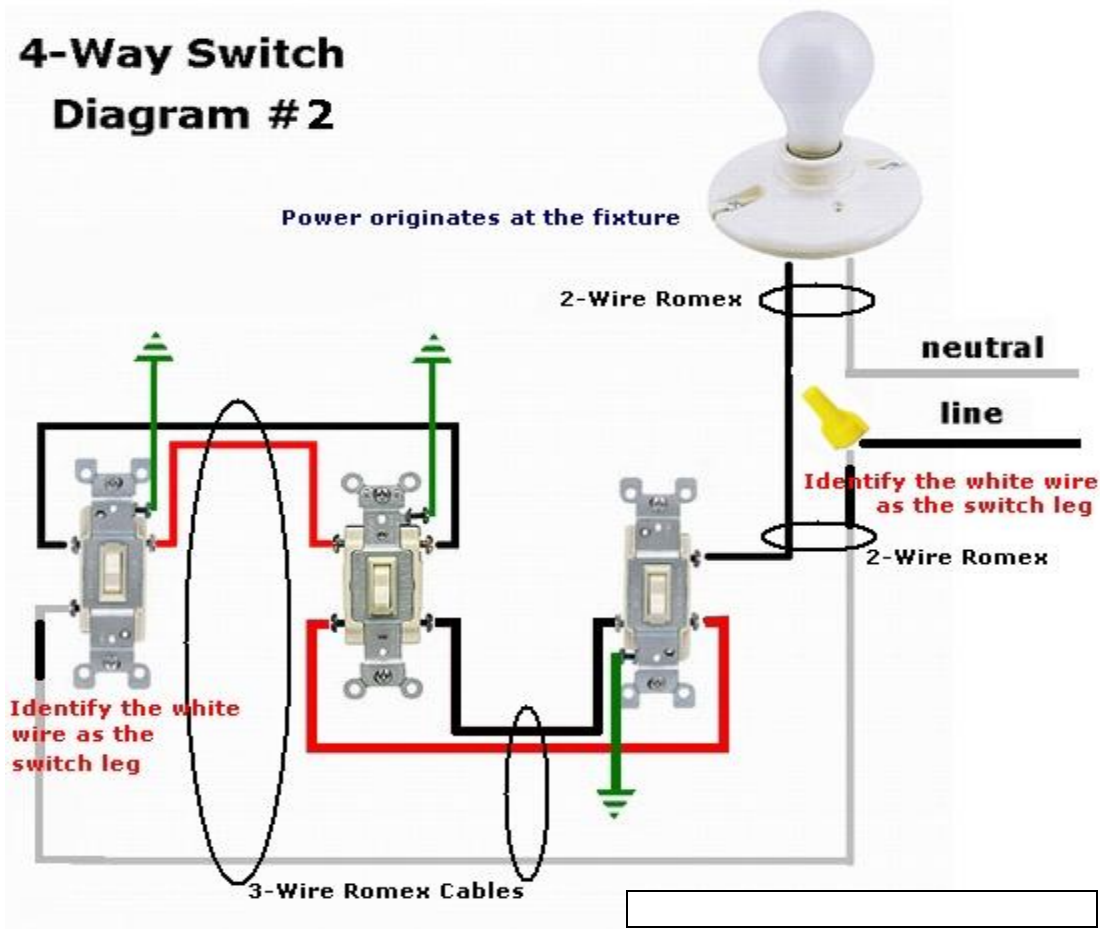Using the diagram below wire the light receptacle to the switches.



Evaluation Score Card

	Possible	Points Earned
Correct Switch	5	_____
Correct wires	5	_____
Properly tightened	5	_____
Project is straight and neatly constructed	3	_____
Safe work habits	2	_____
Total	20	_____